

Ohms Law

There is a direct relationship between current, voltage and resistance. The relationship between current, voltage and resistance can be summed up by a statement known as Ohm's law.

Voltage (E) is equal to amperage (I) times resistance (R): $E = I \times R$

Other forms of the formula are $R = E/I$ and $I = E/R$

In each of these formulas, E is the voltage in volts, I is the current in amps and R is the resistance in ohms.

The basic point to remember is that as the resistance of a circuit goes up, the amount of current that flows in the circuit will go down, if voltage remains the same.

The amount of work that the electricity can perform is expressed as power. The unit of power is the watt (w). The relationship between power, voltage and current is expressed as:

Power (w) is equal to amperage (I) times voltage (E): $W = I \times E$

This is only true for direct current (DC) circuits; The alternating current formula is a tad different, but since the electrical circuits in most vehicles are DC type, we need not get into AC circuit theory.